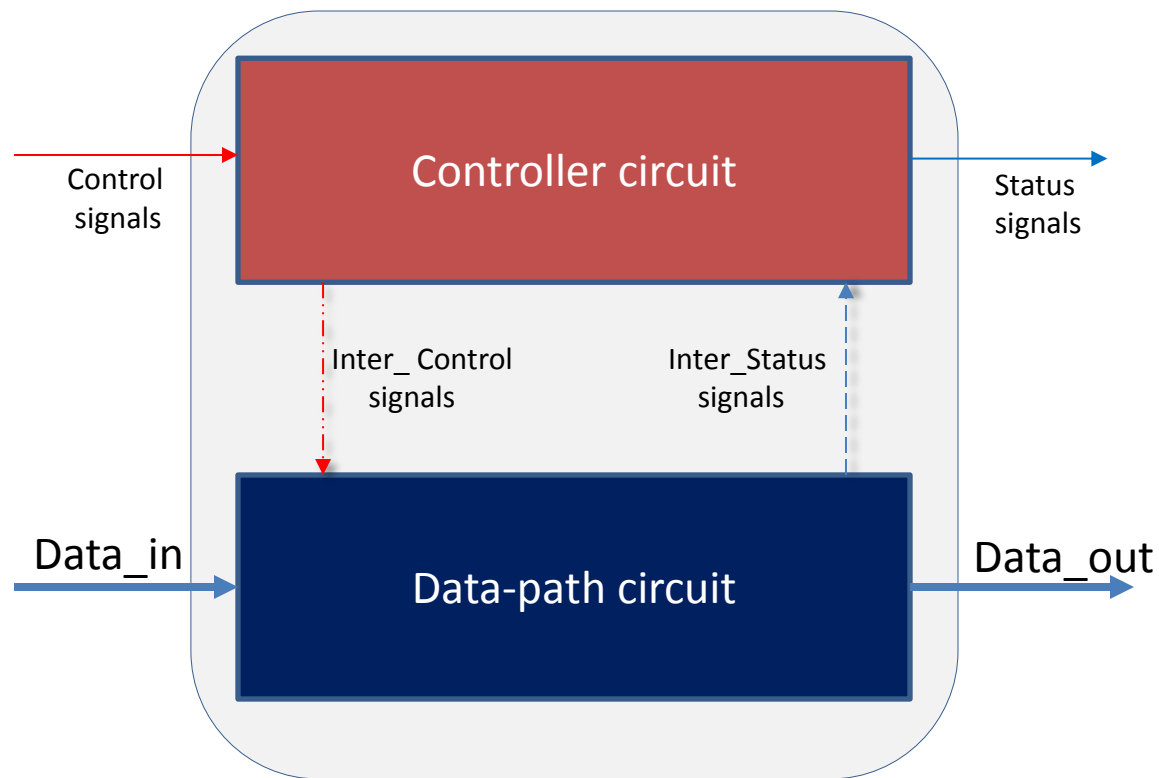


# IC Design

## Lab 2: Bit Counting Circuit

# system have two parts



# Course 2: Bit Counting Circuit

Suppose we want to count the number of '1's in a word. Algorithm to do this:

$B=0$

# While (A # 0) do



if ( $a_0 = 1$ ) then

**B = B+1**


end if

right shift A


End while

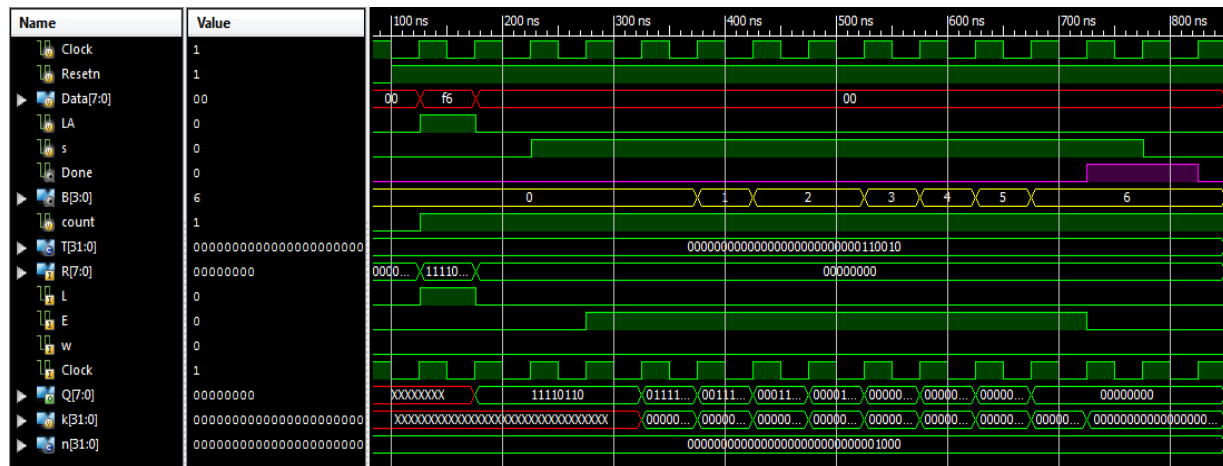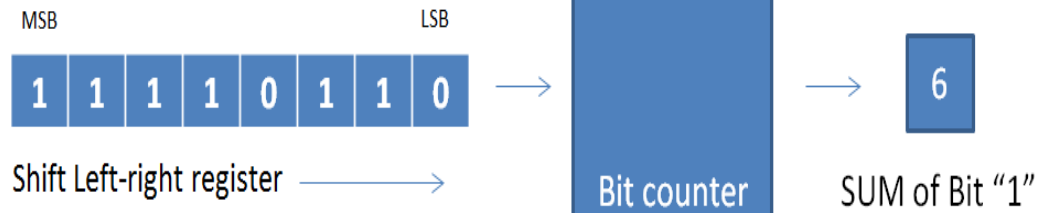


# Bit Counting Circuit

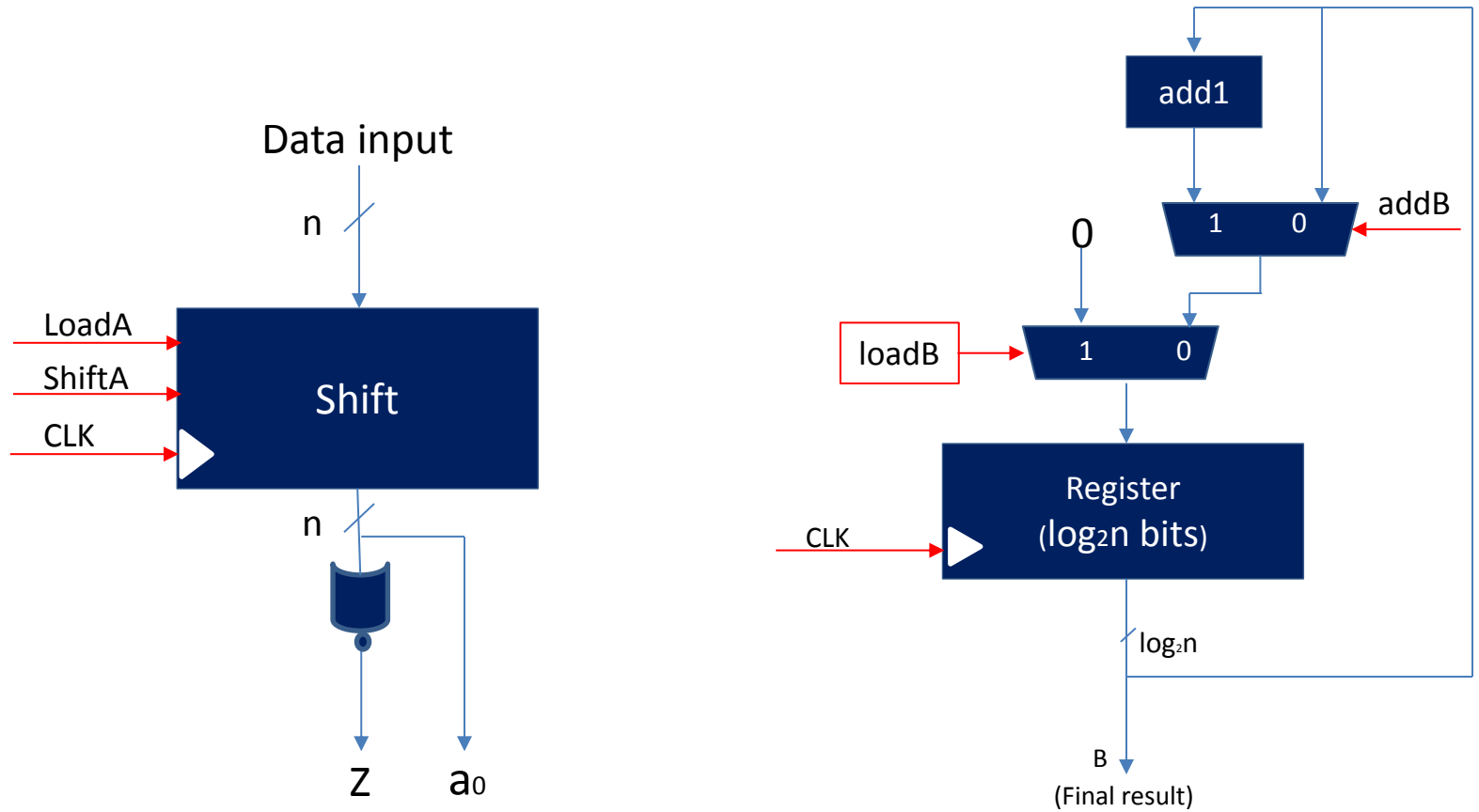

# Bit Counting Circuit\_2

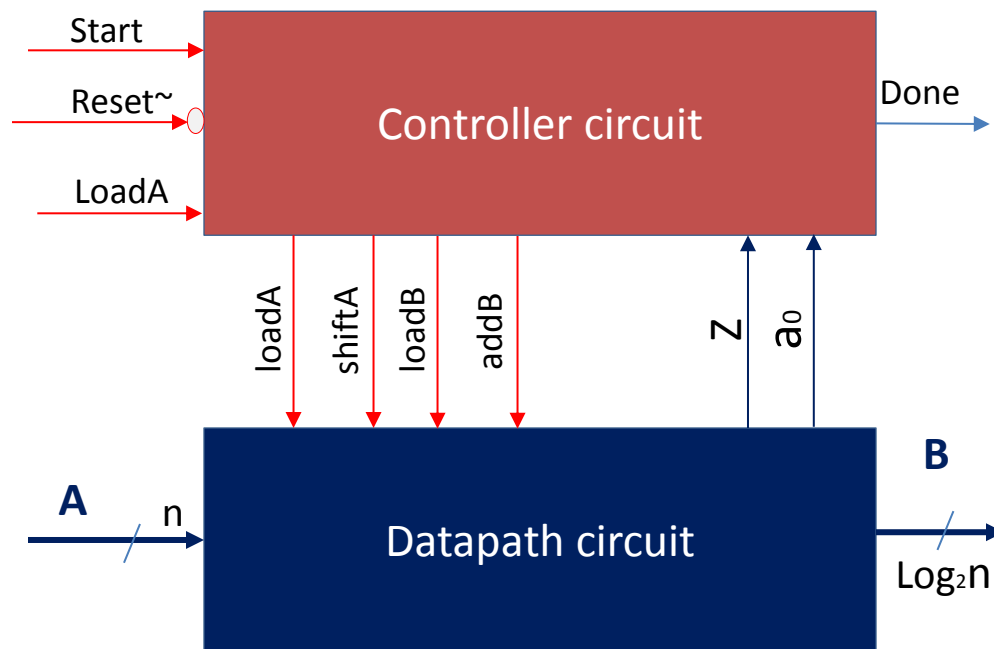

# FSM of Bit Counting Circuit

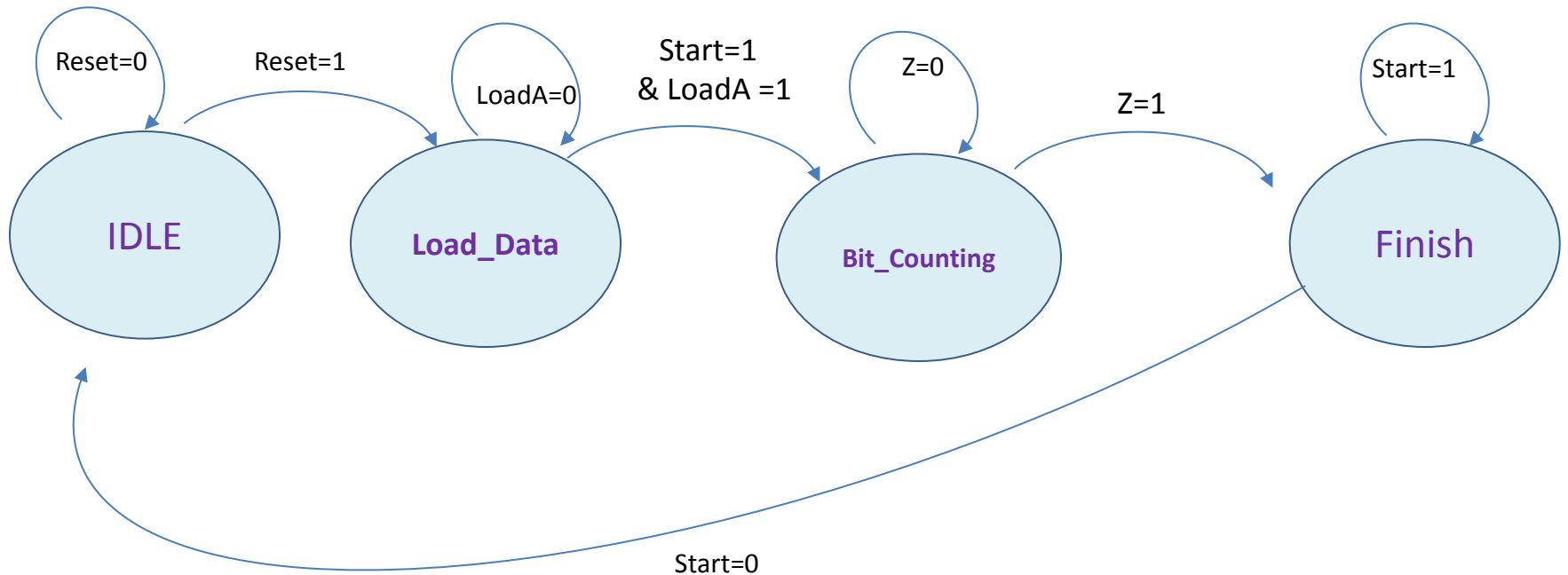

# Exercise Bit\_Counting\_Circuit

Table 4-1: Slider Switch Connections

Switch	SW7	SW6	SW5	SW4	SW3	SW2	SW1	SW0
FPGA Pin	K13	K14	J13	J14	H13	H14	G12	F12

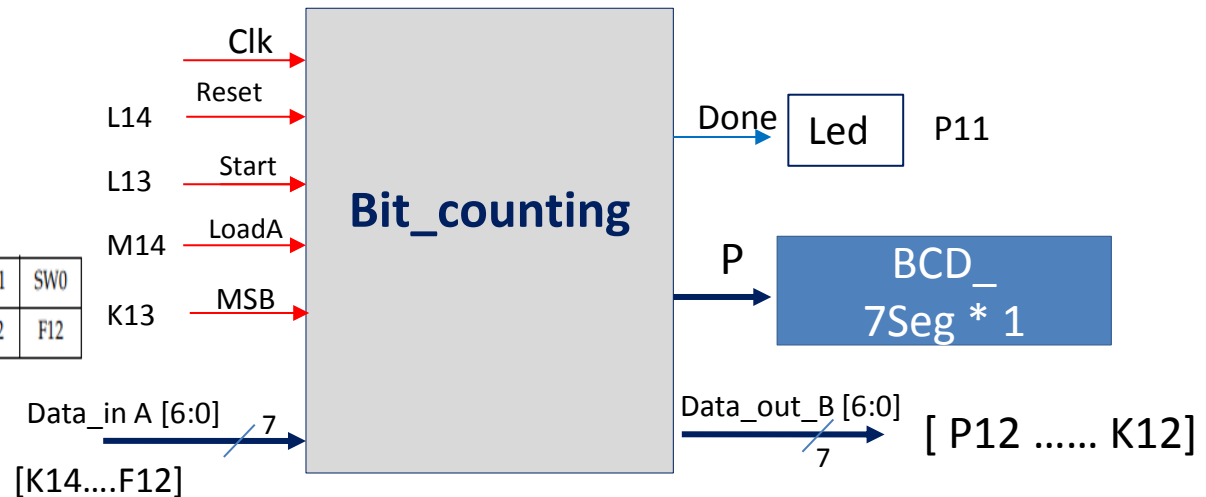


Table 4-2: Push Button Switch Connections

Push Button	BTN3 (User Reset)	BTN2	BTN1	BTN0
FPGA Pin	L14	L13	M14	M13

Table 4-3: LED Connections to the Spartan-3 FPGA

LED	LD7	LD6	LD5	LD4	LD3	LD2	LD1	LD0
FPGA Pin	P11	P12	N12	P13	N14	L12	P14	K12