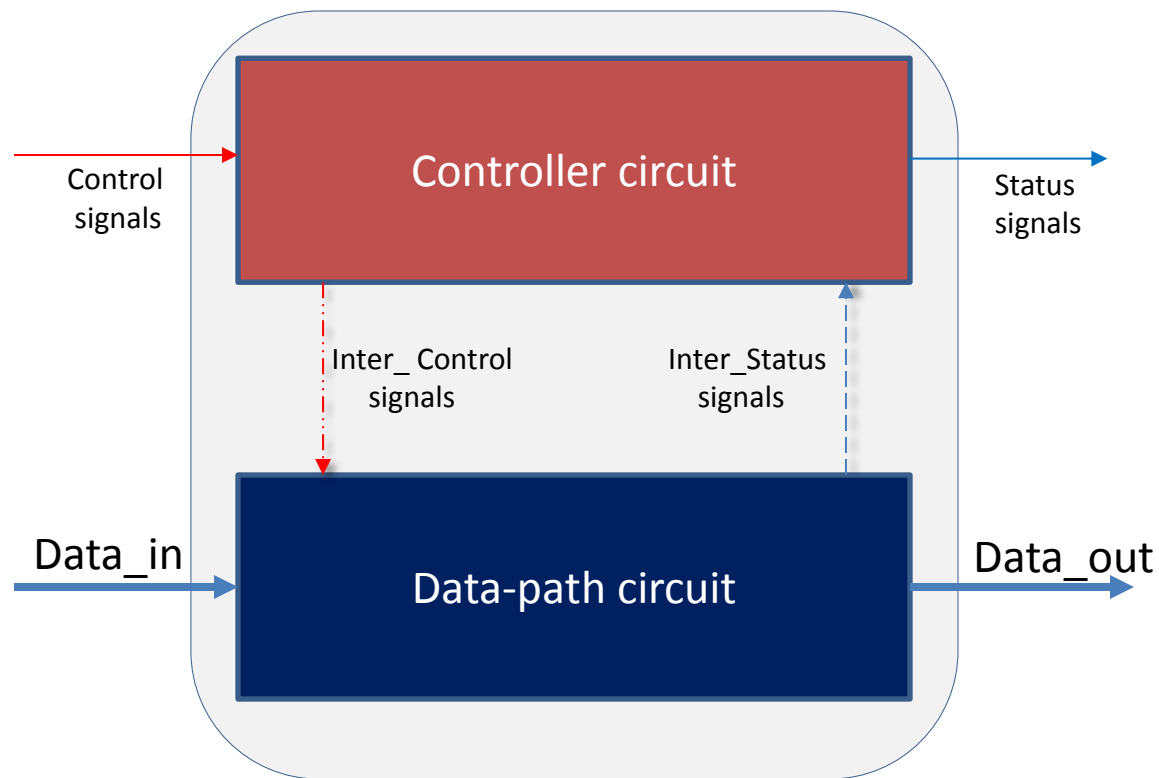


# IC Design

# Simplest systems have two parts




Start out simple

Suppose we want to build a circuit  
to calculate  $X^3$   
(Exponent)

# Start out simple

## Design the $X^3$

### (Exponent)

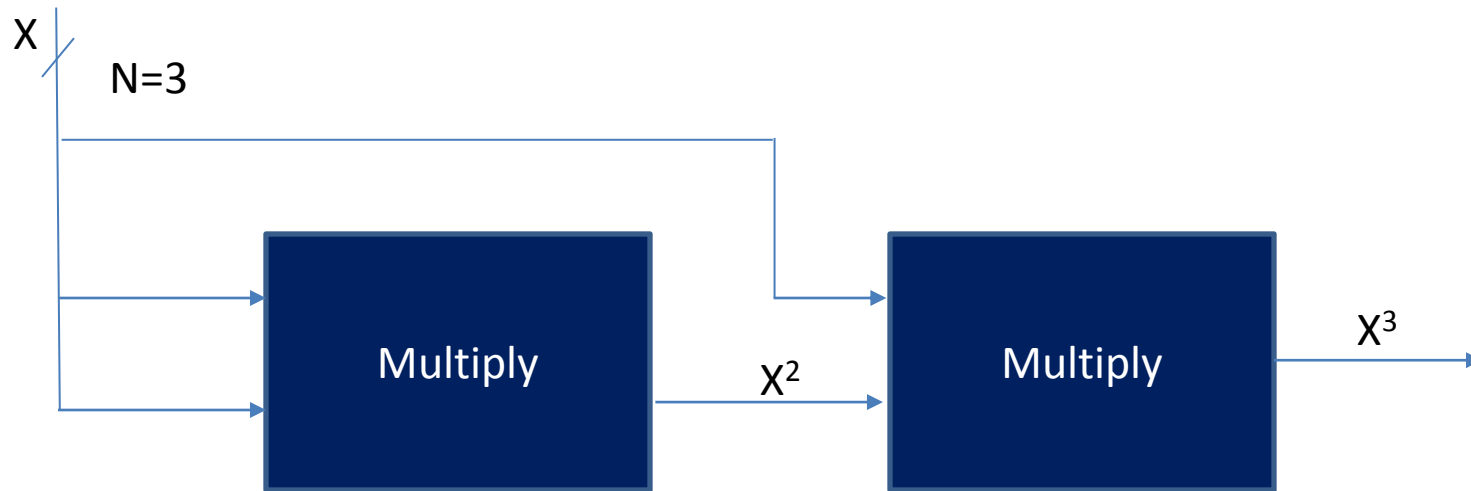


$X^2$

# Start out simple

## Design the $X^4$


(Exponent)

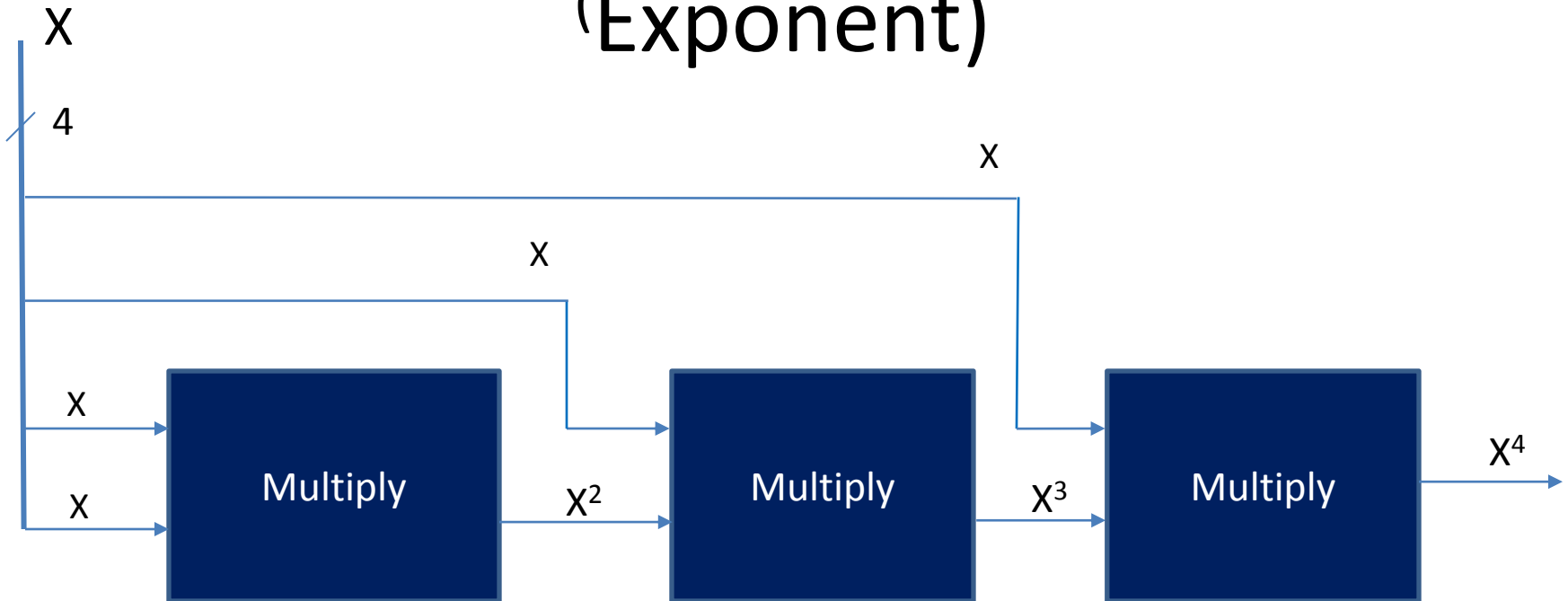

# Start out simple

## Design the $X^n$


(Exponent)

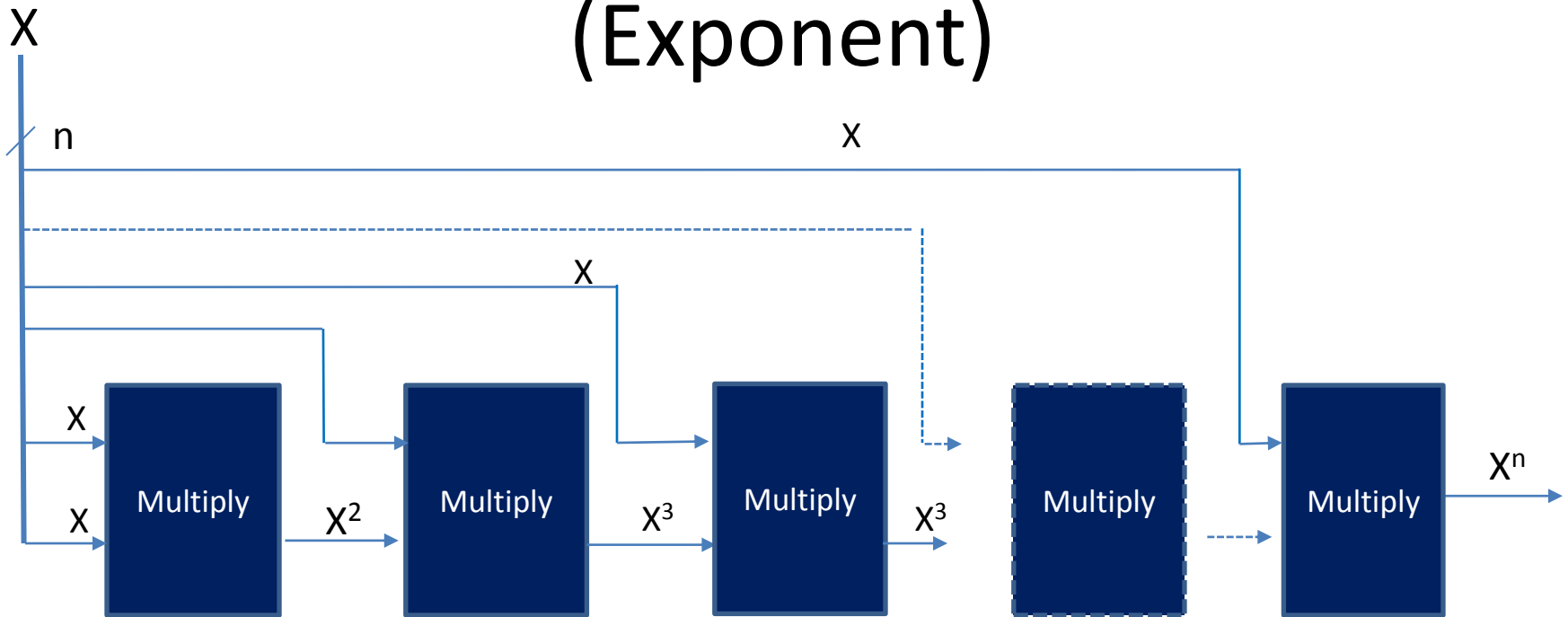

What if we want to compute  $X^A$  where  $X$  and  $A$  are both inputs



# Start out simple

## Design the $X^A$

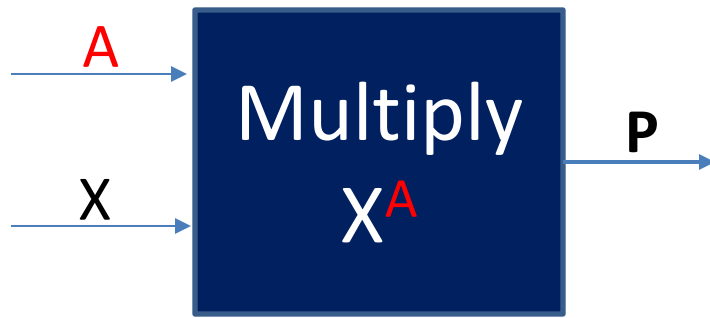


```
P = 1; CNT = A-1;  
while (CNT >= 0) do  
    P = P * X;  
    CNT = CNT - 1;  
end while;
```

# Design the $X^A$

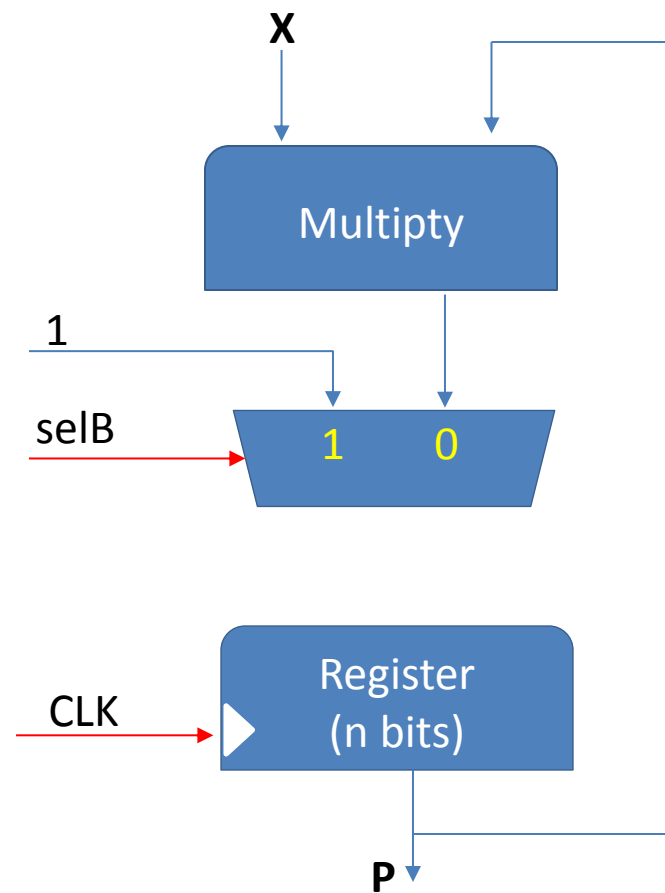
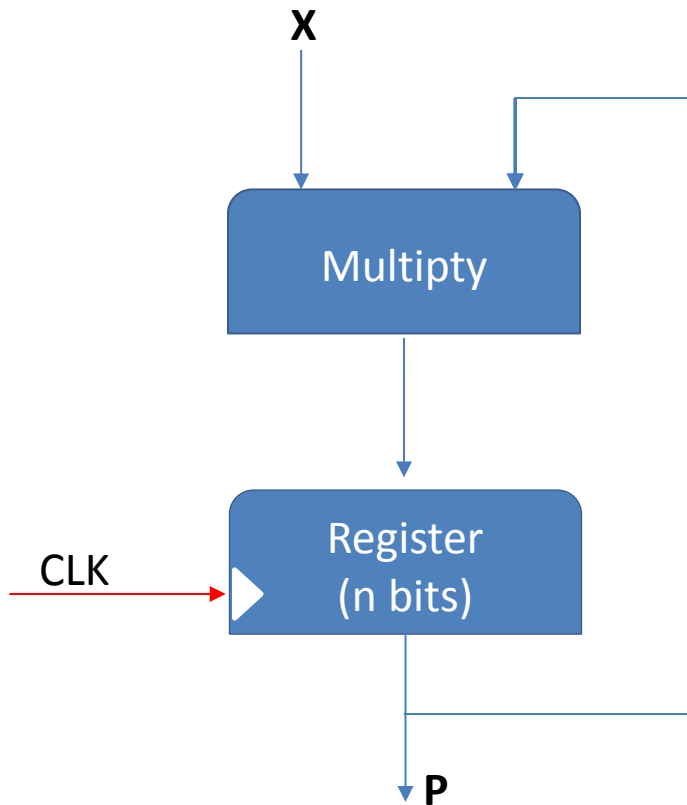






# Design the $X^A$

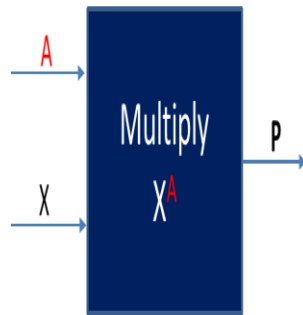
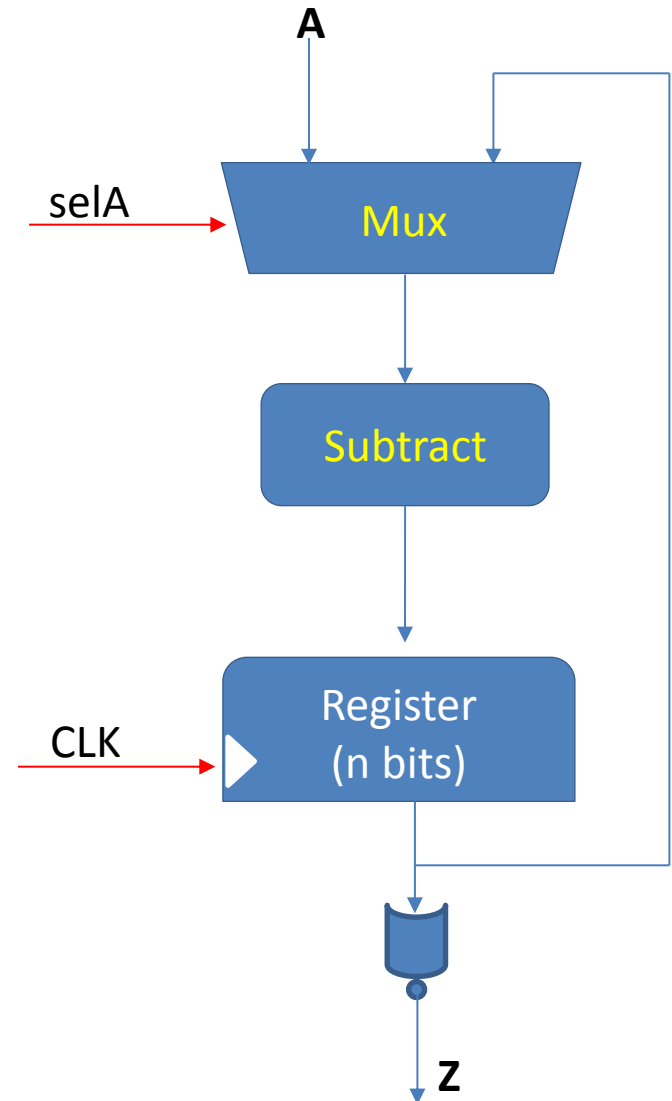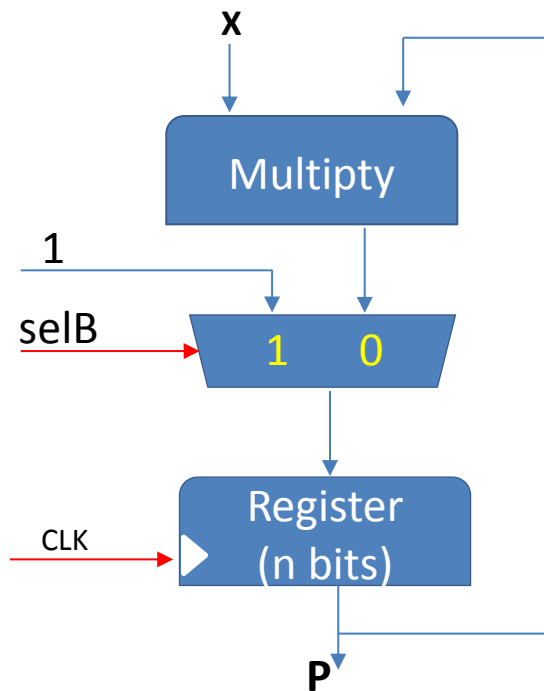
```
P = 1; CNT = A-1;  
while (CNT >= 0) do  
    P = P * X;  
    CNT = CNT - 1;  
end while;
```






# Design the $X^A$

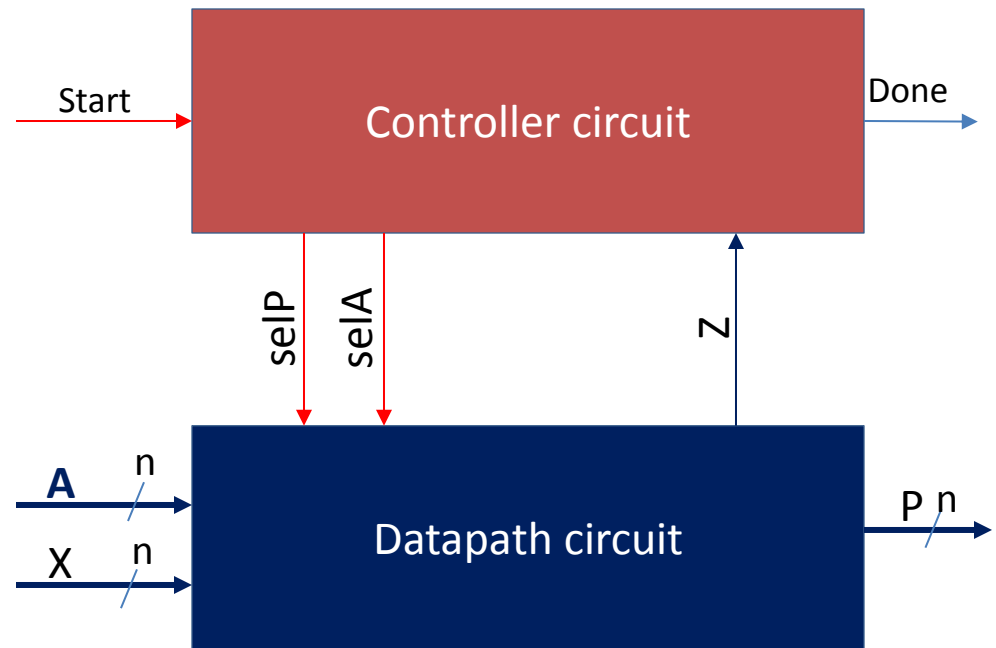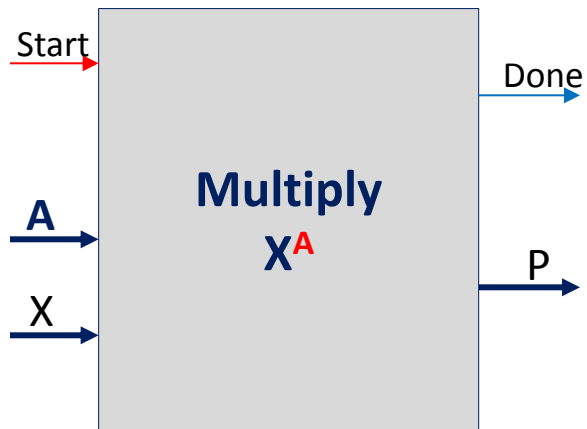


Model of Control Path & Data Path

# Design the $X^A$

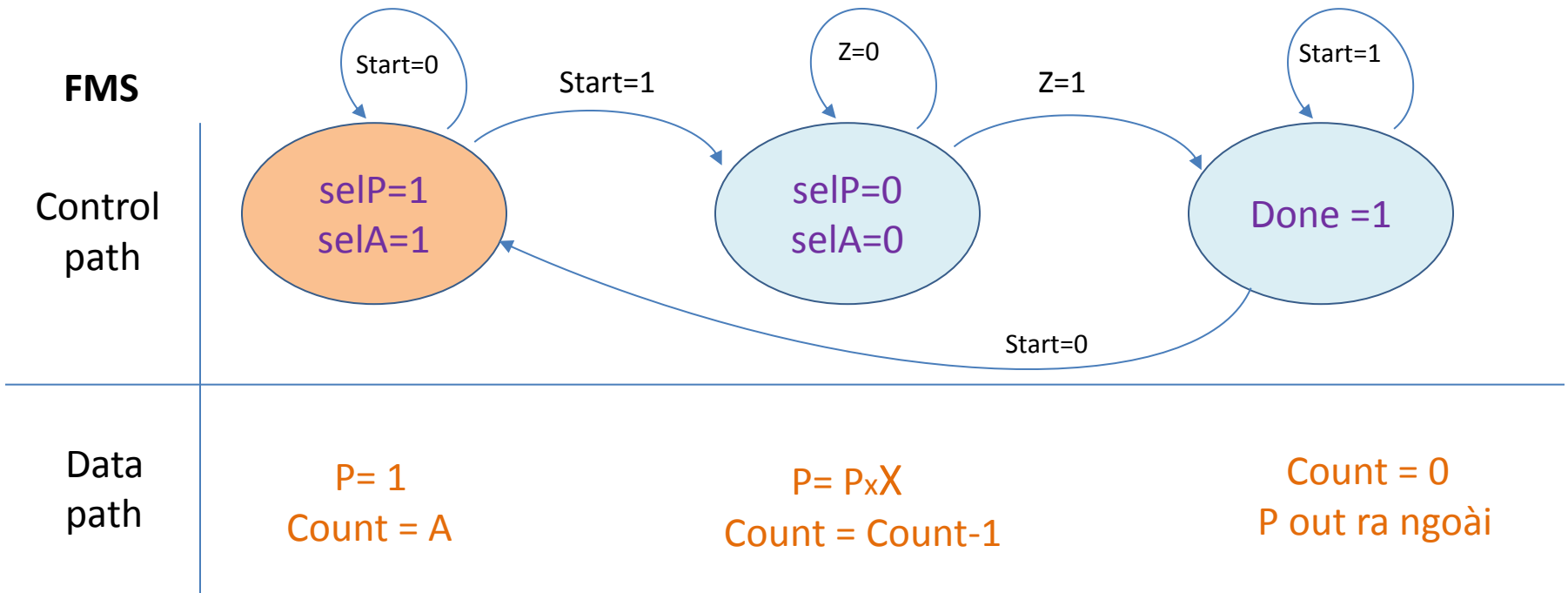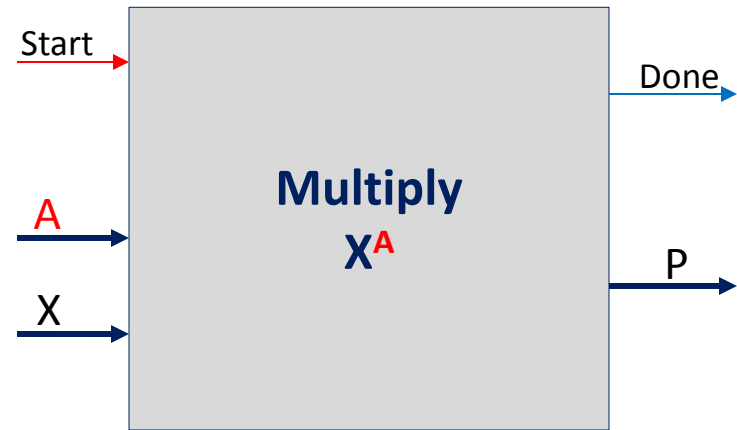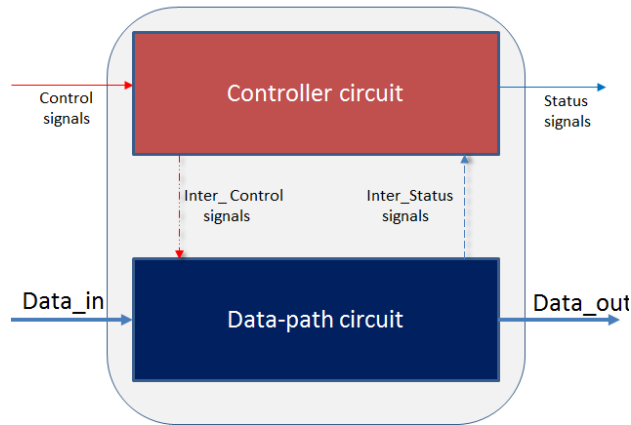

# Implementation on FPGA board

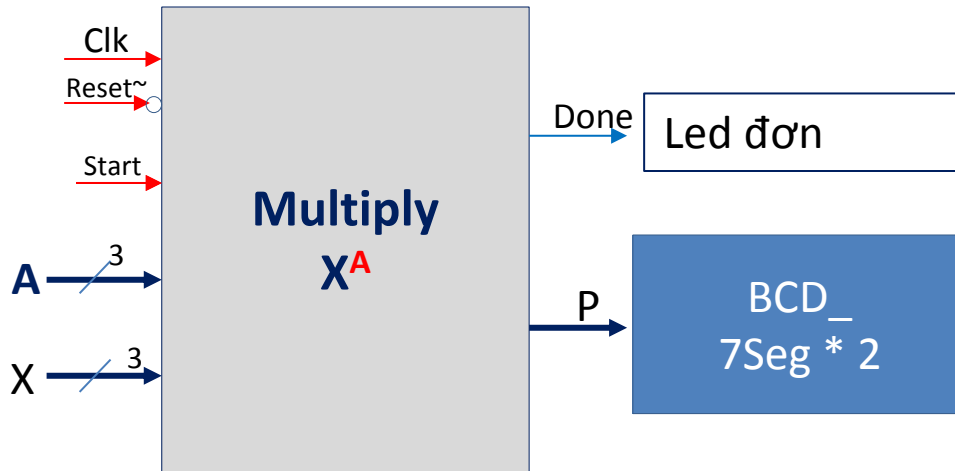

Giải thích thêm:

- Khi Start = 1 : Mạch thực hiện tính toán hàm mũ, giá trị được xuất ra 2 Led 7 đoạn
- Khi có Reset mức âm : đèn Done tắt và 2 Led- 7 đoạn về giá trị '0'
- A được gán từ 2 switch
- X được gán từ 2 switch

Chú ý :

2 switch thể hiện từ 0 – 3 giá trị, do đó hàm mũ này tính tối đa là 81 giá trị ( 3 mũ 3 = 81)

Do mạch chạy nhanh, có thể thêm Delay để thấy giá trị Led 7 đoạn tăng dần

Trong quá trình tính toán : Led Done tắt, khi tính xong Led Done sáng